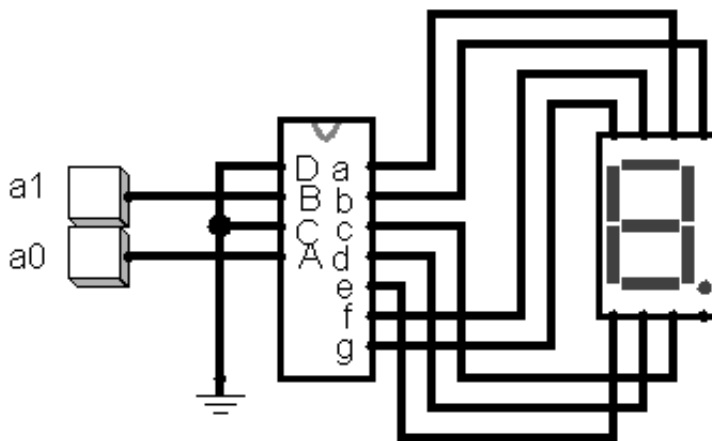


# Lab Report 3

CPE282 Fall 2020

Brennen Green


## BCD to Seven Segment Display



*\* There should be a  $200\ \Omega$  resistor between every pin a-g and the 7-segment display. I could not find this feature in logisim.*


This design went very smoothly and followed my prelab design spot on. One weird thing that came up however was that when I plugged in my *first* 7-segment display it worked initially, got very hot, then started glitching out. I had my lab TA review this and we couldn't find an issue (resistors were being used). We ended up ditching that original display and hooking up a new one and all of the problems were solved! Other than that there were no big issues with this design, it made things a lot simpler than designing a driver by hand. The one thing to note is that my prelab design did have a slight error in that it did not pins D and C on the BCD. We fixed this in my final design.

## Black Box Logic

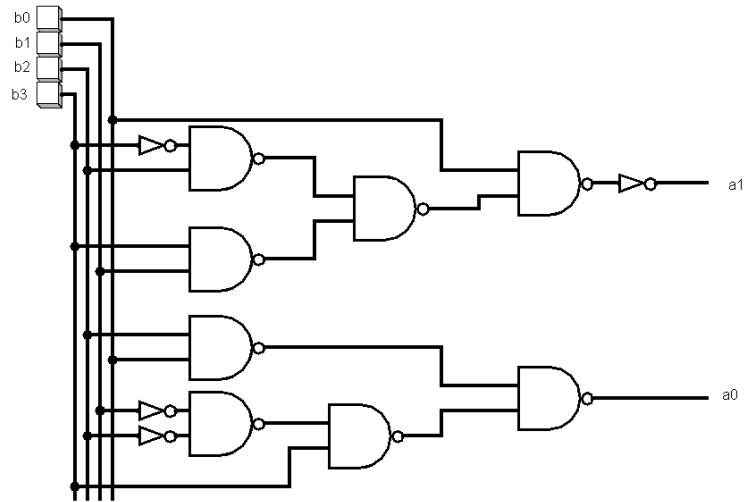

Once again this design went really smoothly. After having discovered the amazing use of the 74LS04 inverter chip last lab wiring these circuit up became a lot easier. I didn't have to deviate from my prelab design what so ever. However, it was noted that there is a more optimal solution if the goal were to be as optimal as possible.

## Final Design

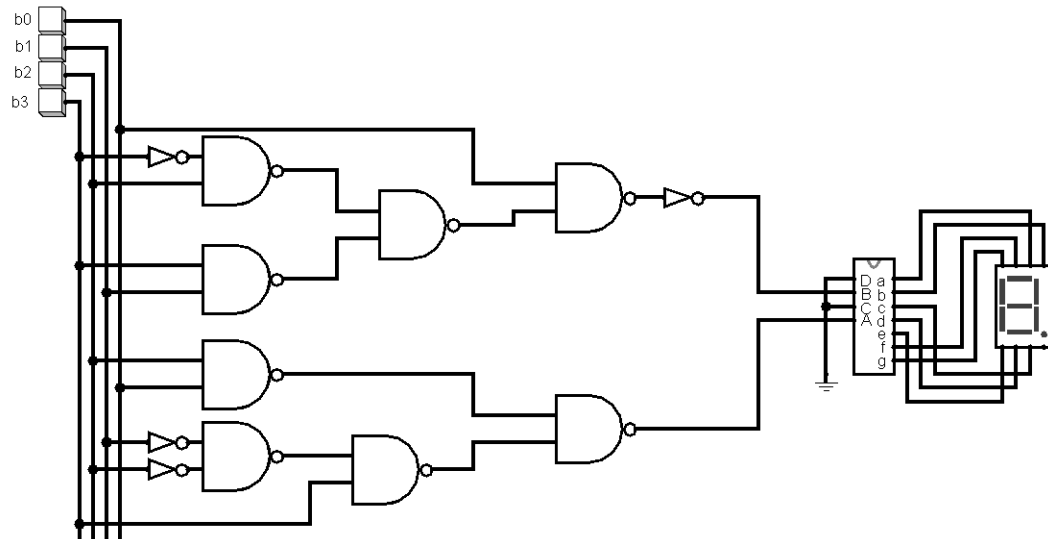

In all this lab went really smoothly and I enjoyed it. Despite the weird event that occurred with my 7-segment display burning me originally everything else went according to plan. I've discovered that these integrated circuits such as the BCD make life a lot easier!